


# Chapter 14, Part 2

Dr. Eric Becker

CS 4341

Fall 2017

# The Traffic Light Problem

 



# The Traffic Light Problem

- Description
  - Reset-North-south is green light, east-west is red light.
  - carew=1 means a car is detected coming from east or west. Start the sequence to change North-South to red, and east-west to green
  - A green light must change to a yellow light before changing to a red light
  - A green light can only be present if the perpendicular direction is a red light

# The Traffic Light Problem: State Table

State	One-Hot	Car East-West	Next State	North-South Lights (green-yellow-red)	East-West Lights (green-yellow-red)
<b>GNS (Green North-South)</b>	<b>0001</b>	<b>0</b>	<b>GNS</b>	(100)	(001)
<b>GNS</b>	<b>0001</b>	<b>1</b>	<b>YNS</b>	(100)	(001)
YNS (Yellow North-South)	0010	0	GEW	(010)	(001)
YNS	0010	1	GEW	(010)	(001)
GEW (Green East-West)	0100	0	YEW	(001)	(100)
GEW	0100	1	YEW	(001)	(100)
YEW (Yellow East-West)	1000	0	GNS	(001)	(010)
YEW	1000	1	GNS	(001)	(010)


# The Traffic Light Problem

 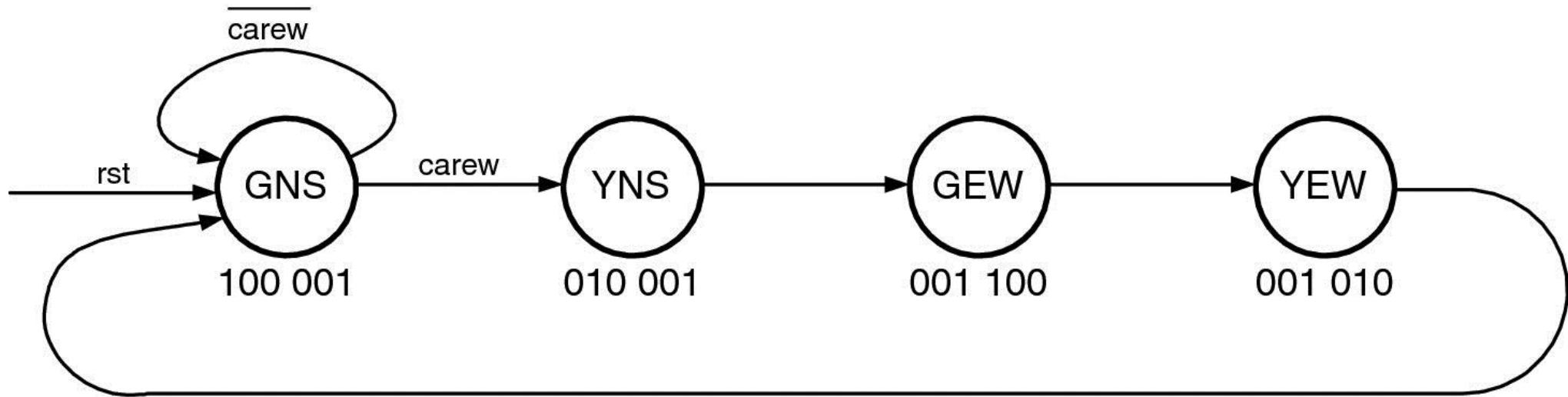

# The Traffic Light Problem

- Actual state is the *state variable*, as a digital encoded number
- Actual Binary Values to the FSM
  - One-hot notation for the state
  - One-bit notation for the car arriving east-west
  - Three-bit notation for the north-south lights as green-yellow-red
  - Three-bit notation for the east-west light as green-yellow-red.
- 00010100001 for  
Green North, South, Red East West, No car approaching, green light north-south, red light east-west.
 
# A 4-bit Traffic Light Problem: A Circuit




# Implementation of Finite State Machines

- Use a multiple flip-flops.
- A set of multiple Flip Flops (D Flip Flops) is called a *register*.
- And a *state register* is using the flip-flops to record the current state.
  - Hey, look! We've found a memory variable!
- One flip-flop per state.
  - For example, 4 states, 4 flip-flops, and its one-hot...only one flip-flop at a time will be equal to one.



# The D Flip Flop?

 

```
module DFF(clk,in,out);  
    parameter n=1;//width  
    input clk;  
    input [n-1:0] in;  
    output [n-1:0] out;  
    reg [n-1:0] out;  
  
    always @(posedge clk)  
        out = in;  
endmodule
```

# A 2-Bit Traffic Light Example

State	carew	Next	Comment	Light Pattern
00	0	00	GNS, carew=0	NS=(100) EW=(001)
00	1	01	GNS, carew=1	NS=(100) EW=(001)
01	0	11	YNS, carew=0	NS=(010) EW=(001)
01	1	11	YNS, carew=1	NS=(010) EW=(001)
11	0	10	GEW, carew=0	NS=(001) EW=(100)
11	1	10	GEW, carew=1	NS=(001) EW=(100)
10	0	00	YEW, carew=0	NS=(001) EW=(010)
10	1	00	YEW, carew=1	NS=(001) EW=(010)

# Why 2 bit? Easier K-Mapping!

Next State, MSB

<u>carew</u> \S1S0	00	01	11	10
0	0	1	1	0
1	0	1	1	0

MSB=XX1

MSB=s0

Next State, LSB

<u>carew</u> \S1S0	00	01	11	10
0	0	1	0	0
1	1	1	0	0

LSB=X01 V 10X

LSB=  $\sim s1s0 + \text{carew}\sim s1$

LSB=  $(\sim s1)(\sim s0 + \text{carew})$

LSB=  $(\overline{s1}) \wedge (s0 \vee \text{carew})$

# What about the Lights?

State	NS Red	NS Yellow	NS Green
00	0	0	1
01	0	1	0
10	1	0	0
11	1	0	0

Normal form will be simple.

$$\text{NS Red} = (s1 \wedge \overline{s0}) \vee (s1 \wedge s0) = s1$$

$$\text{NS Yellow} = (\overline{s1}) \wedge (s0)$$

$$\text{NS Green} = (\overline{s1}) \wedge (\overline{s0})$$

State	EW Red	EW Yellow	EW Green
00	1	0	0
01	1	0	0
10	0	1	0
11	0	0	1


Normal form will be simple.

$$\text{EW Red} = (\overline{s1} \wedge \overline{s0}) \vee (\overline{s1} \wedge s0) = \overline{s1}$$

$$\text{EW Yellow} = (s1) \wedge (\overline{s0})$$

$$\text{EW Green} = (s1) \wedge (s0)$$

And the circuit would be...

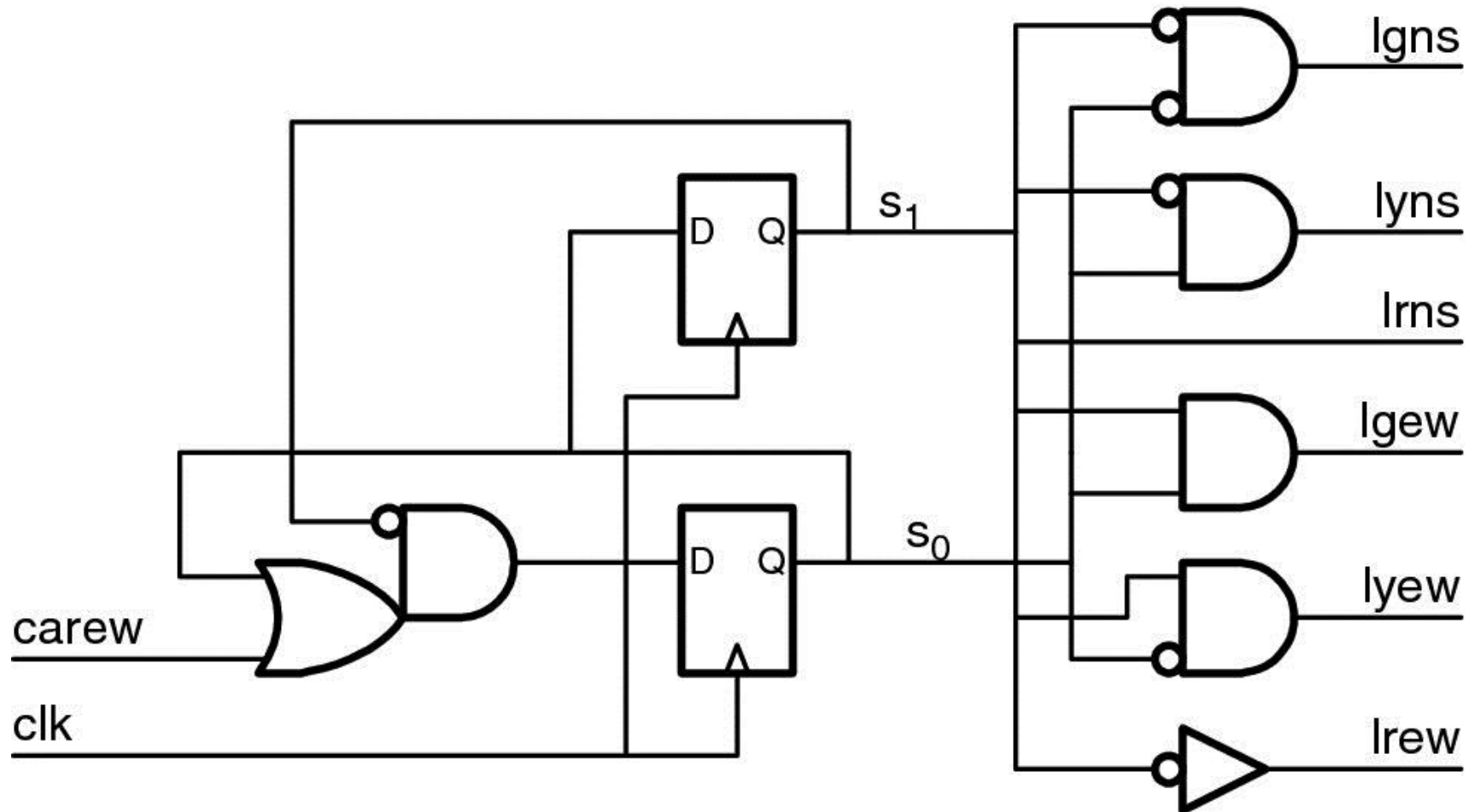

# Verilog

```
//-----  
//  define  states  
//-----  
`define GNS 2'b00  
`define YNS 2'b01  
`define GEW 2'b11  
`define YEW 2'b10  
`define SWIDTH 2 //2Bit
```

```
//-----  
//  define  output codes  
//-----  
`define GNSL 6'b100001  
`define YNSL 6'b010001  
`define GEWL 6'b001100  
`define YEWL 6'b001010
```

# Verilog

```
// Traffic_Light
// Inputs:
//   clk - system clock
//   rst - reset - high true
//   carew - car east/west - true when car is waiting in east-
west direction
// Outputs:
//   lights - (6 bits) {gns, yns, rns, gew, yew, rew}
// Waits in state GNS until carew is true,
// then sequences YNS, GEW, YEW and back to GNS.
//-----
module Traffic_Light(clk, rst, carew, lights) ;
    input clk ;
    input rst ;           // reset
    input carew ;         // car present on east-west road
    output [5:0] lights ; // {gns, yns, rns, gew, yew, rew}
    wire [`SWIDTH-1:0] state, next ; // current and next state
    reg [`SWIDTH-1:0] next1 ;       // next state w/o reset
    reg [5:0] lights ;              // output - six lights 1=on

    // instantiate state register
    DFF #(`SWIDTH) state_reg(clk, next, state) ;
    // next state and output equations - this is combinational logic
```

```
always @(*) begin
    case(state)
        `GNS: {next1, lights} = {(carew ? `YNS : `GNS), `GNSL} ;
        `YNS: {next1, lights} = `{GEW, `YNSL} ;
        `GEW: {next1, lights} = `{YEW, `GEWL} ;
        `YEW: {next1, lights} = `{GNS, `YEWL} ;
        default: {next1, lights} = `{SWIDTH+5{1'bx}};
    endcase
end
// add reset
assign next = rst ? `GNS : next1 ;
endmodule // Traffic_Light
```

# Verilog

```
module Test_Fsm1 ;
    reg clk, rst, carew ;
    wire [5:0] lights ;

    Traffic_Light tl(clk, rst, carew, lights) ;

    // clock with period of 10 units
    initial begin
        clk = 1 ; #5 clk = 0 ;
        forever
            begin
                $display("%b %b %b %b", rst, carew,
tl.state, lights ) ;
                #5 clk = 1 ; #5 clk = 0 ;
            end
        end

    // input stimuli

    initial begin
        rst = 0 ; carew=0 ;
        #15 rst = 1 ; carew = 0 ; // reset
        #10 rst = 0 ; // remove reset
        #20 carew = 1 ; //car arrives
        #30 carew = 0 ; // car leaves
        #20 carew = 1 // car comes and stays
        #60 // 6 more cycles
        $stop ;
    end
endmodule
```