

Sequential Circuits


Dr. Eric Becker

CS 4341

Fall 2017

Sequential Circuits

 - Sequential Circuits have Feedback.
- Output depends on current input
- AND the history of previous inputs
- This feedback is referred to as the *state*.
- $out = f(in, state)$
- $q_{new} = \bar{r} \wedge (s \vee q_{old})$




Sequential Circuits

- This is a flip-flop
- The logic may denote the circuit change
- But the value is depended on the input history.
- If R is true, then block is reset.
- If R is false, Depends on S and Previous State.
- This is a flip-flop

Qold	R	S	Qnew
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

Sequential Circuits


 
- q starts off at an unknown state
- When r resets (goes high), q will fall to 0 at t_1
- When S becomes a high input at t_2 , q will go to 1
- At t_3 , reset again.
- After reset, and S is high, Q remains high until reset
- Q remembers its value
- This is called a *timing diagram*



Synchronous Sequential Circuits

- The signal for the state change can occur at any time
- These are referred to as races
- For now, sequential circuits are *synchronous* with a control clock
- State changes are only on the clock signal, and this allows sequential circuits to behave as *finite state machines*. (FSM)

Synchronous Sequential Circuits

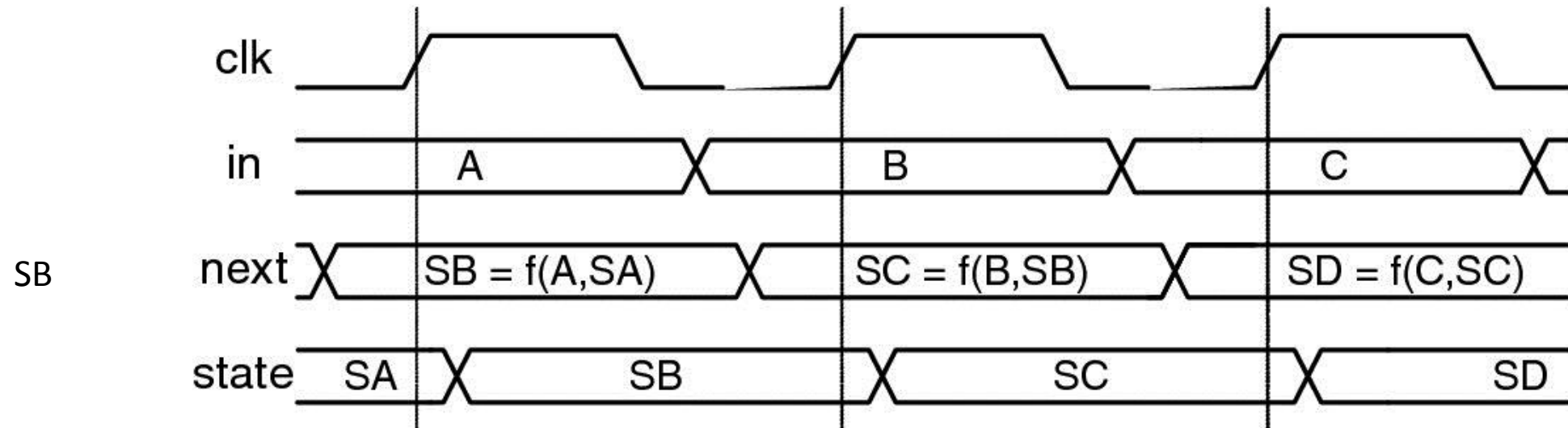 

Synchronous Sequential Circuits


- This means that a circuit can handle a regular expression
- Can it recognize a sequence?
- Give a cycle (clock), and a set of states, can it recognize a pattern?

14.2

Clk	State	In	Out
0	00	0	0
1	00	1	0
2	01	1	0
3	11	0	0
4	01	1	0
5	11	1	0
6	10	0	0
7	11	1	0
8	10	1	1
9	00		0

A State Table

A State Diagram

 

Each circle is a state with a label.

00 is the start state.

Each arrow is a transition

The numerator is the input signal

The denominator is the output signal

In this case, four 1,1,1,1 yields 0,0,0,1

What other patterns would be recognized?

Are there any?