


# Factoring Finite-State Machines


# Factoring Finite-State Machines


- Splitting a larger, complex FSM
  - Into two or more smaller, less complex FSM
- Each state of the sub-machine represents one dimension or factor of the larger machine
- For example, One portion can be data, the other can be control

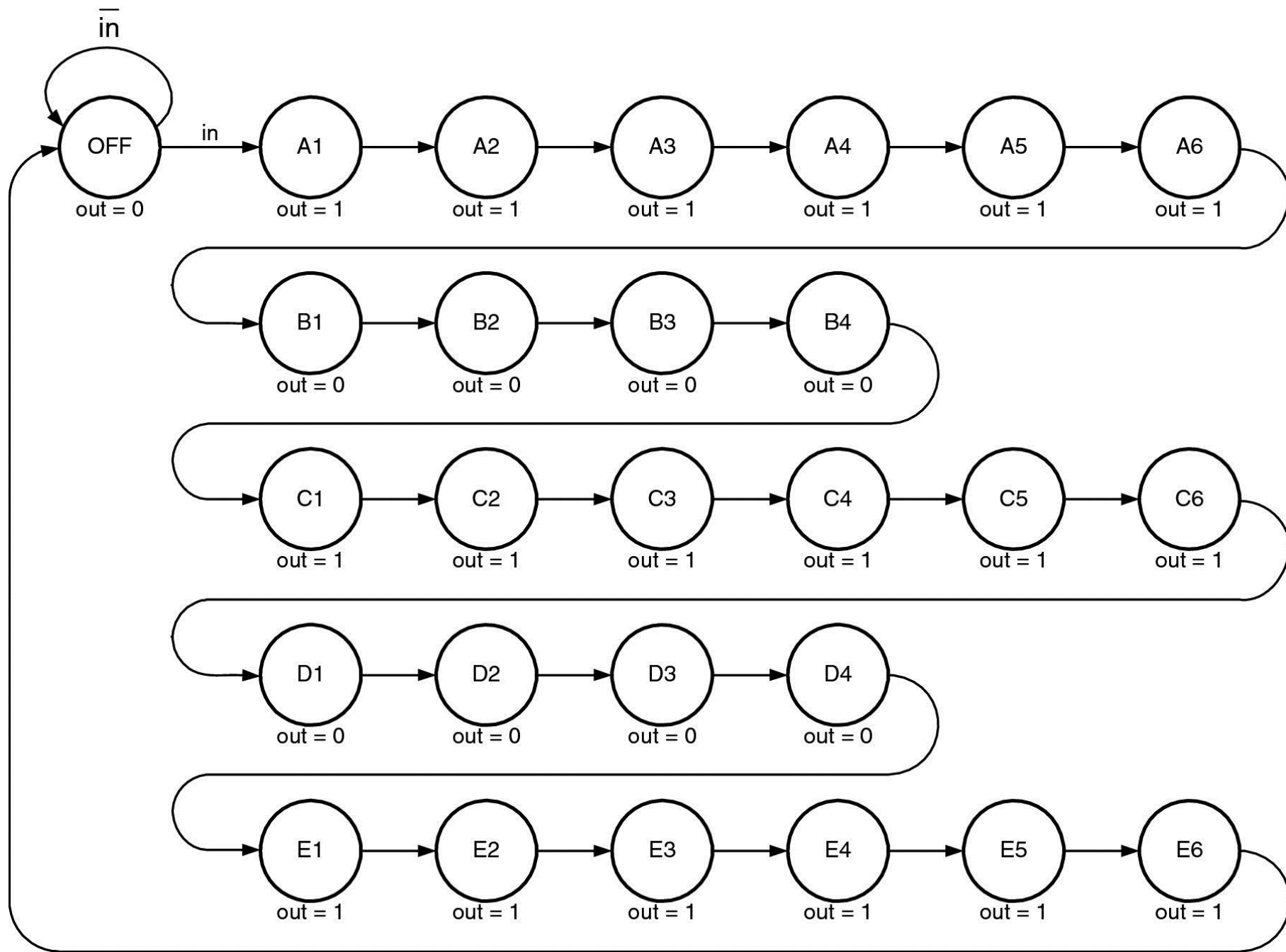
# Example 1: Flashing Light


- Single input in
- Single output out (LED)
- Starts at OFF state
- LED hot for Six Cycles
- LED dark for four cycles
- LED hot for six cycles
- LED dark for four cycles
- LED hot for six cycles
- Returns to OFF



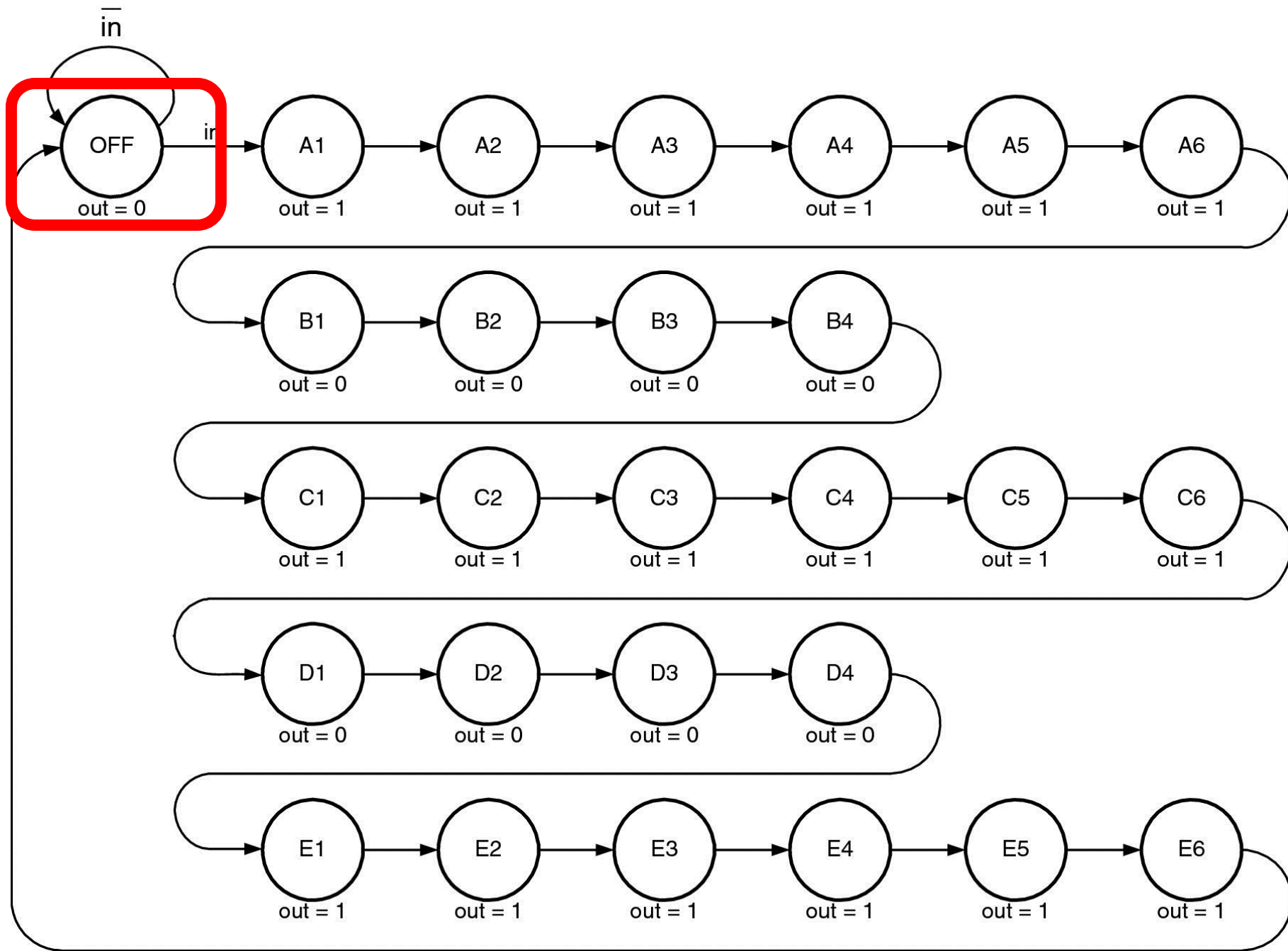


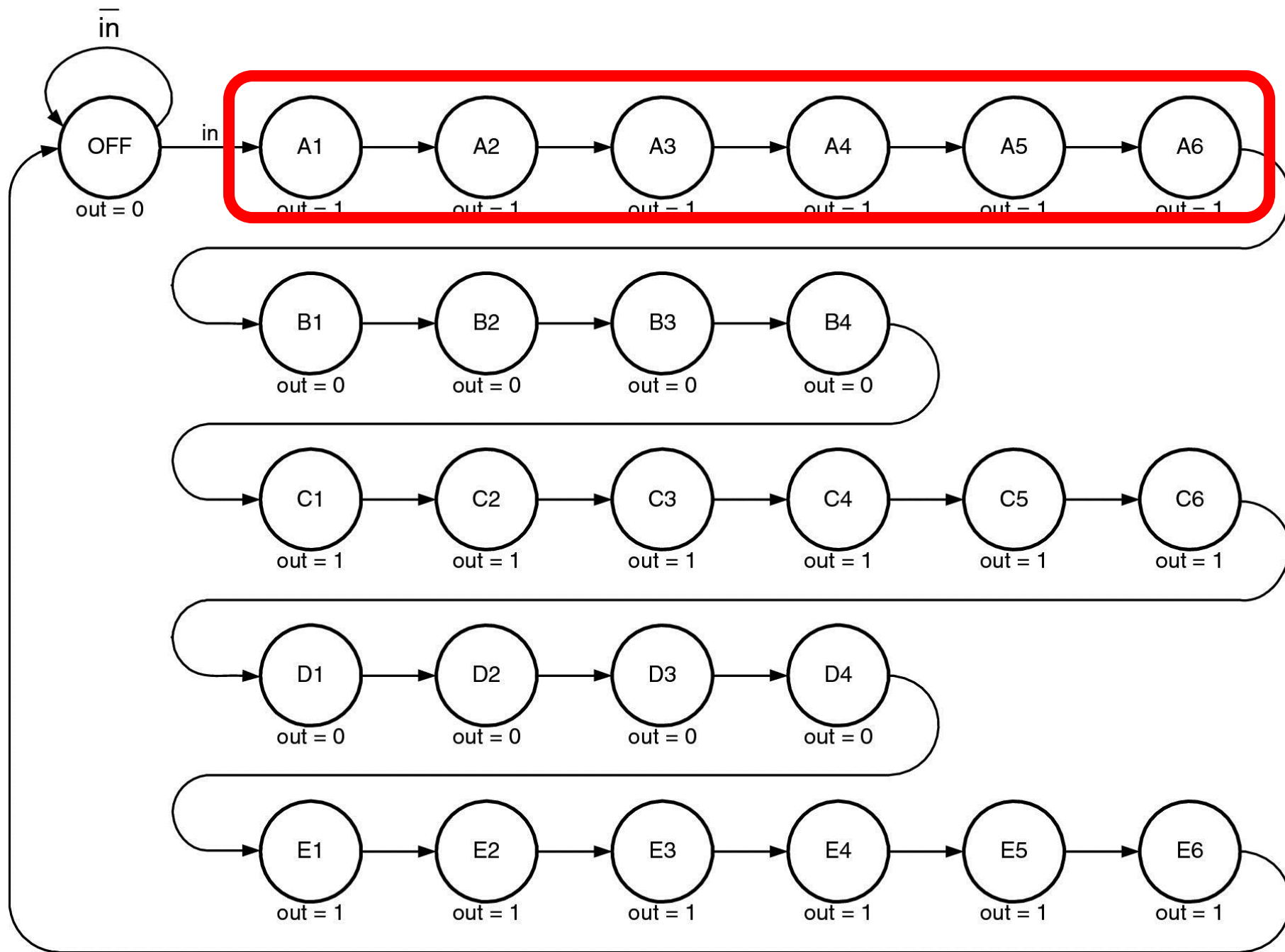


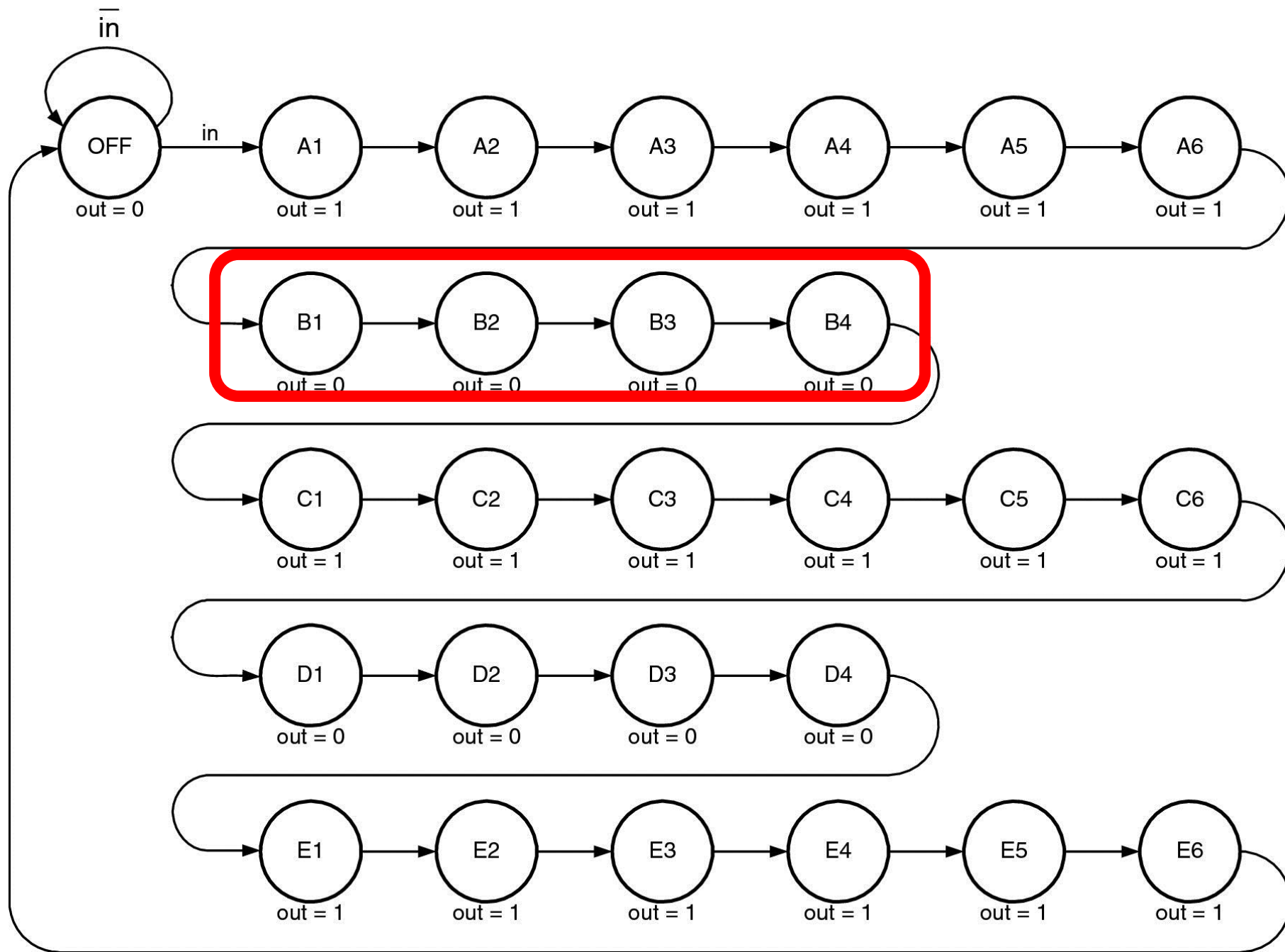

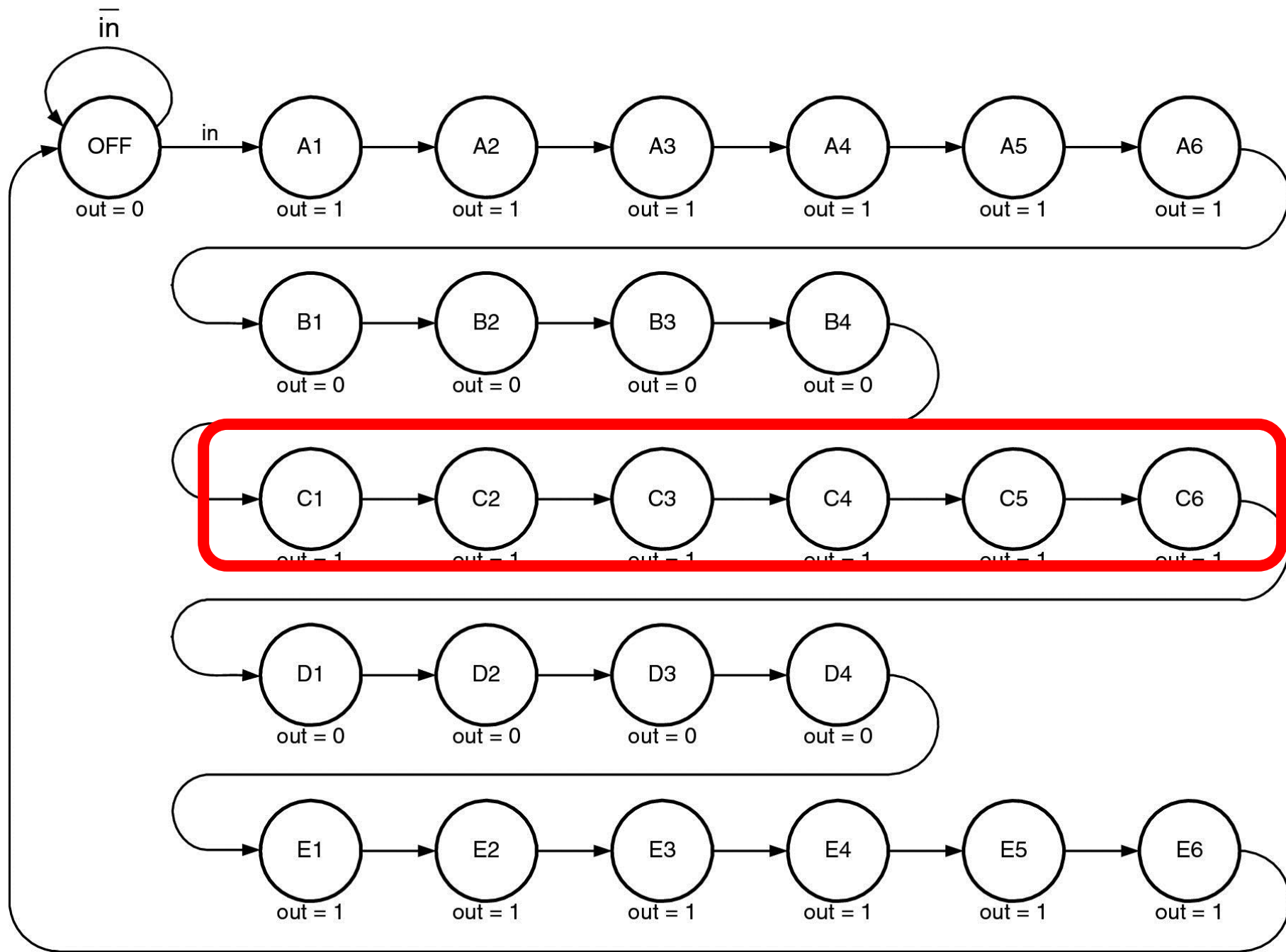



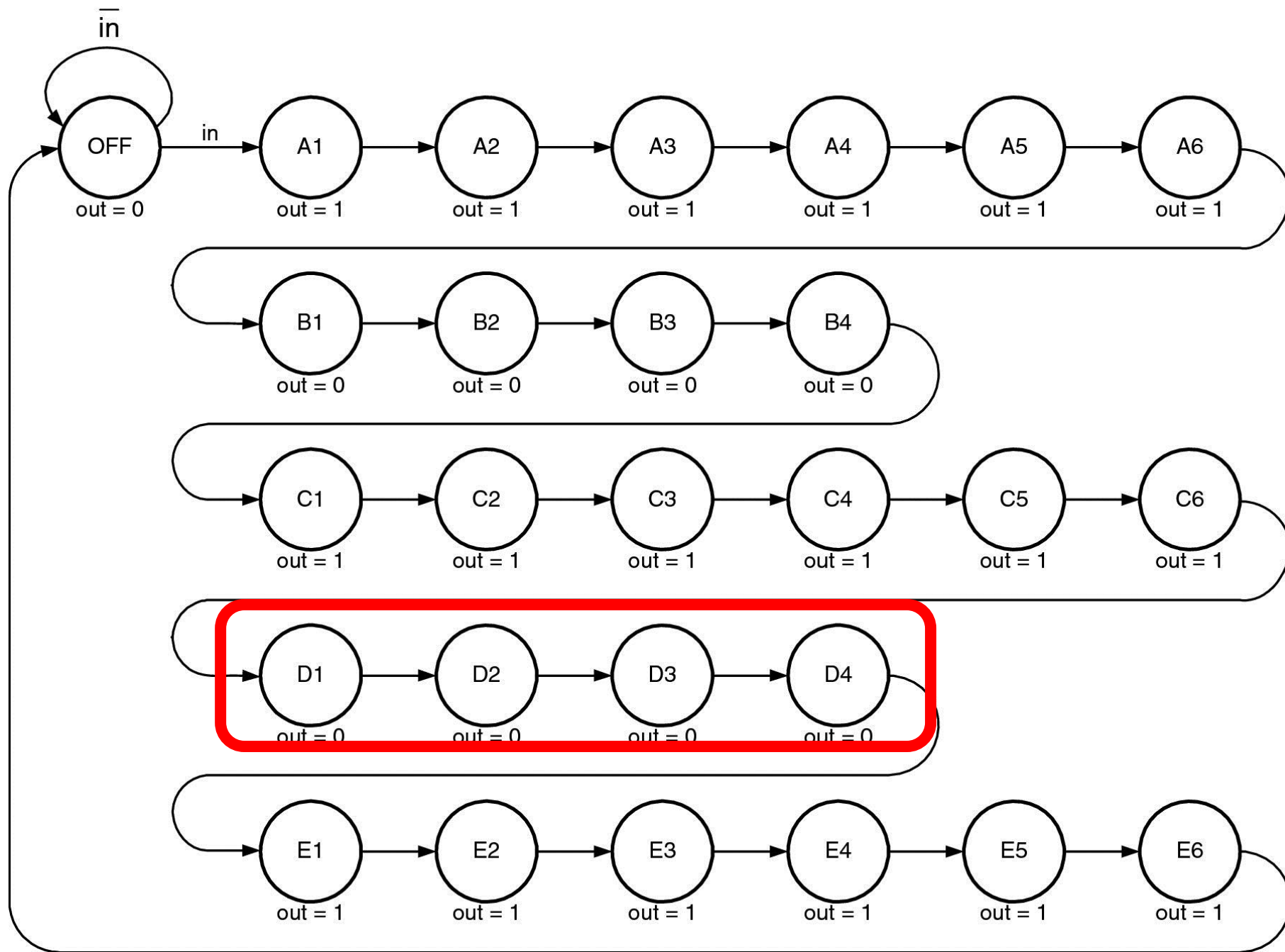

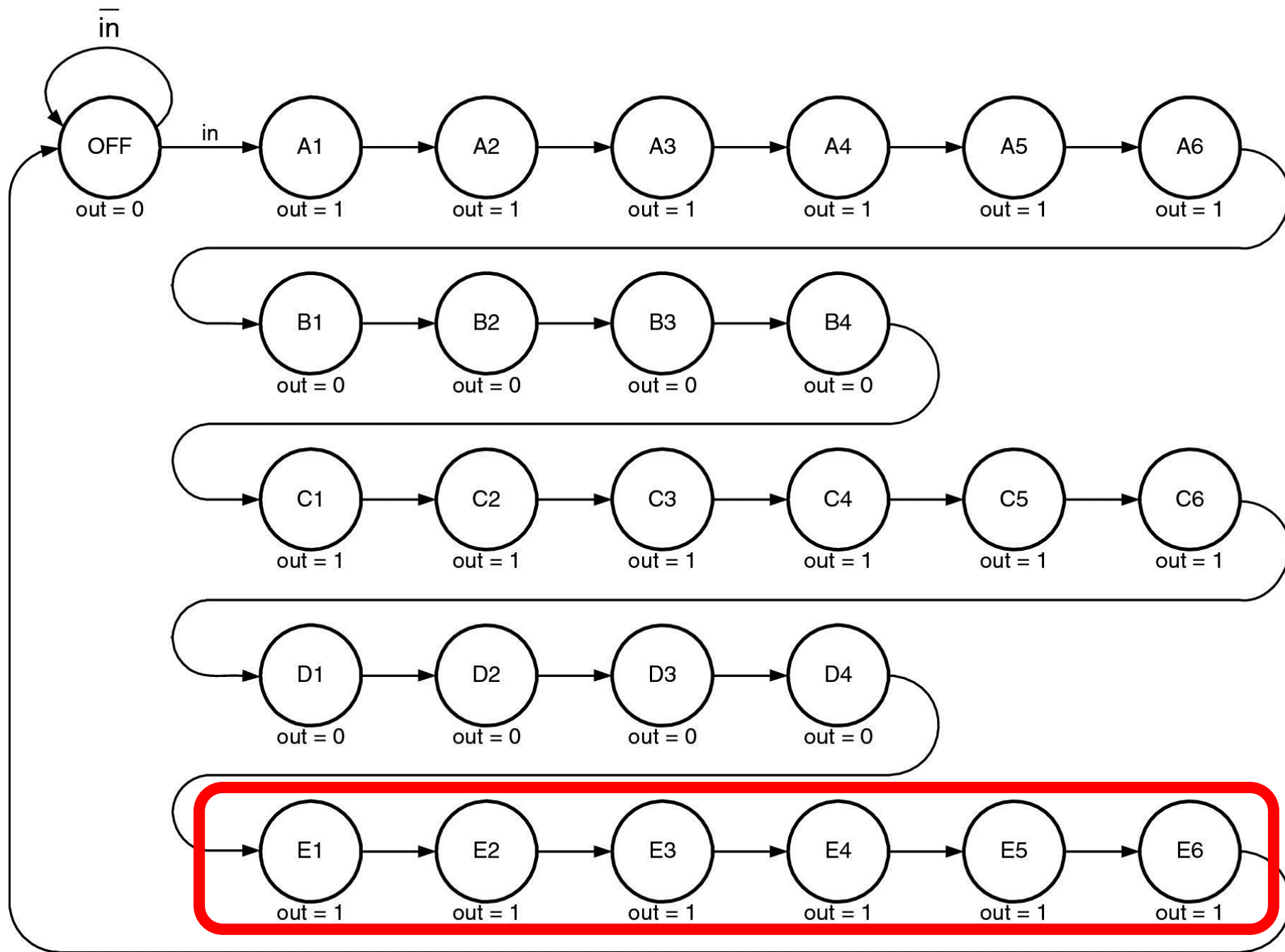


# Example 1: Flashing Light

- Workable
- But is not Simple, and is rather Stupid
- Ideal state machines should have as few parts as possible
- Ideal state machines should have as few decisions as possible
- The state machine is a single, long chain.
- To change the timing, the entire state machine would have to be rewritten.

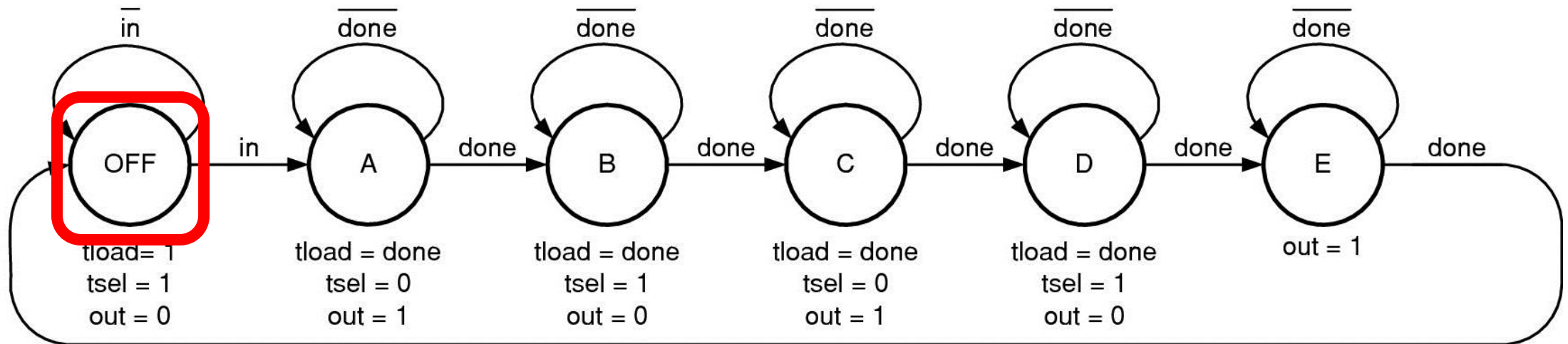
# Example 1: Flashing Light

- First, add a Timer with a Load (Chapter 16) to each of the on-off parts of the flash.



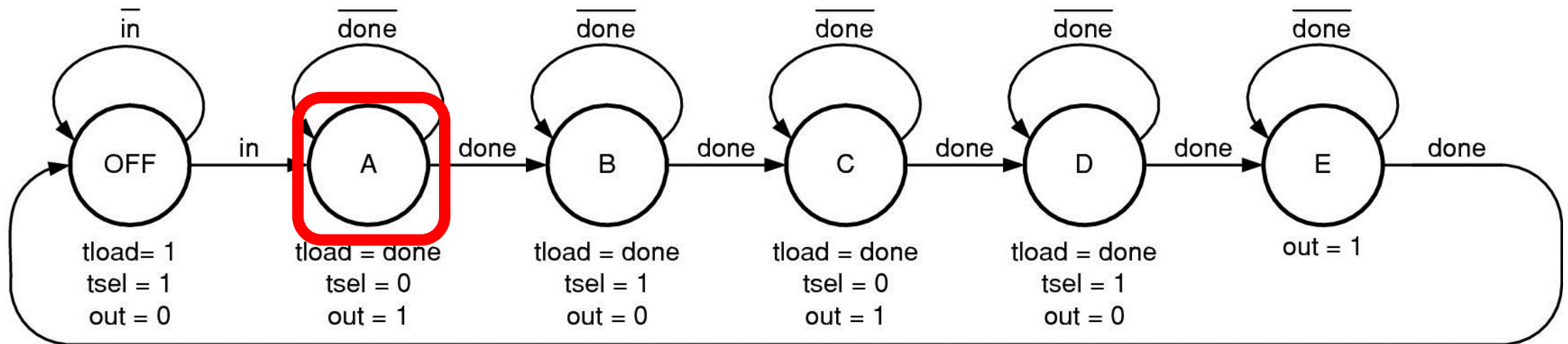
# Example 1: Flashing Light

- First, add a Timer with a Load (Chapter 16) to each of the on-off parts of the flash.



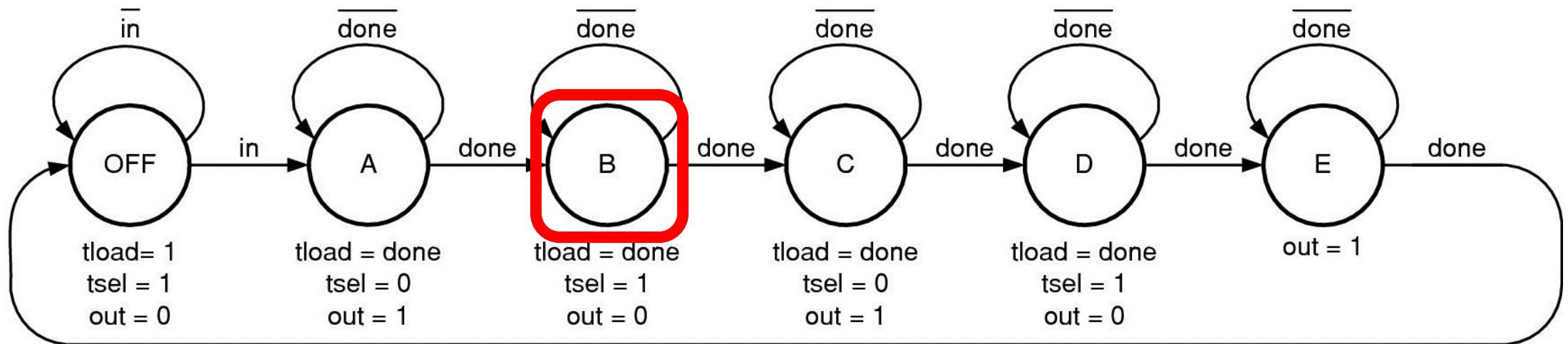
# Example 1: Flashing Light

- First, add a Timer with a Load (Chapter 16) to each of the on-off parts of the flash.



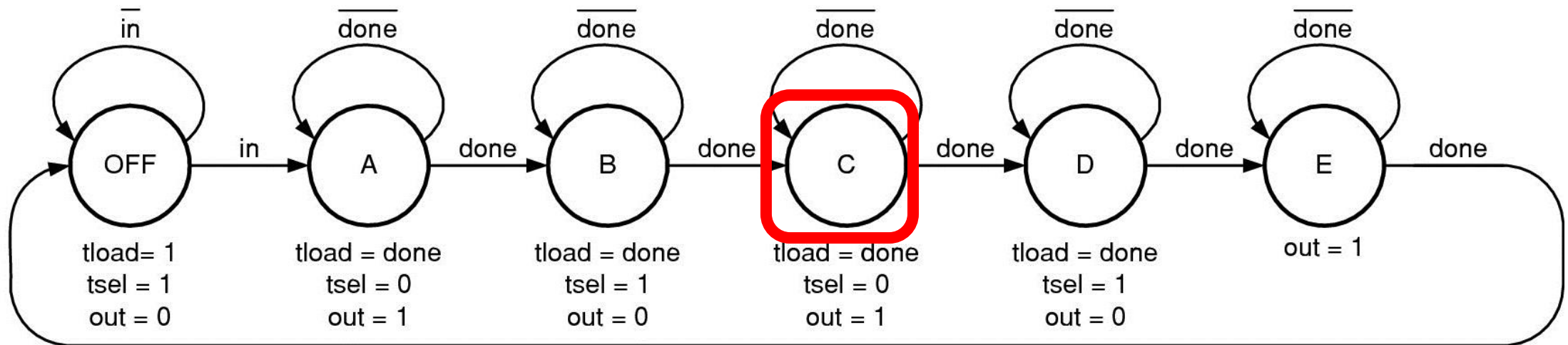
# Example 1: Flashing Light

- First, add a Timer with a Load (Chapter 16) to each of the on-off parts of the flash.


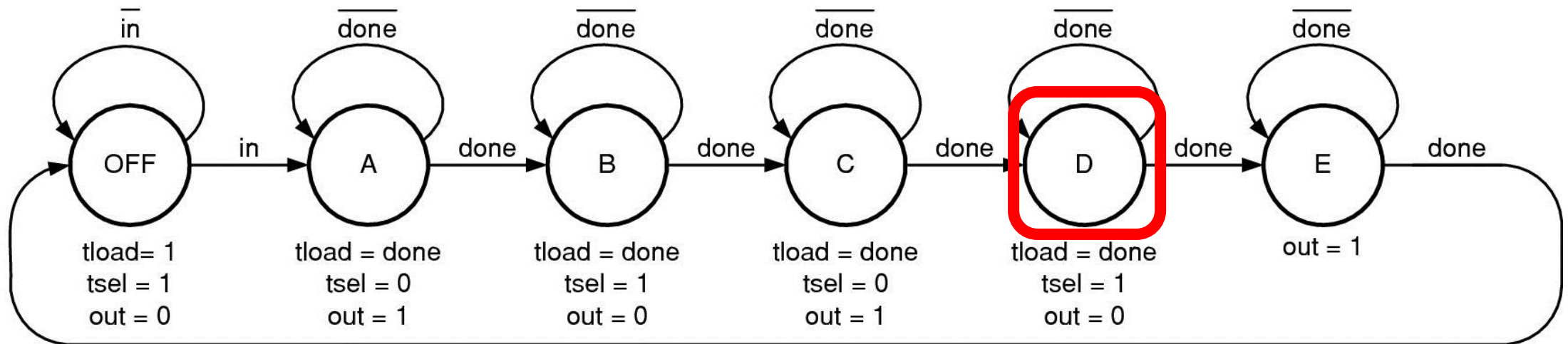
# Example 1: Flashing Light


- First, add a Timer with a Load (Chapter 16) to each of the on-off parts of the flash.





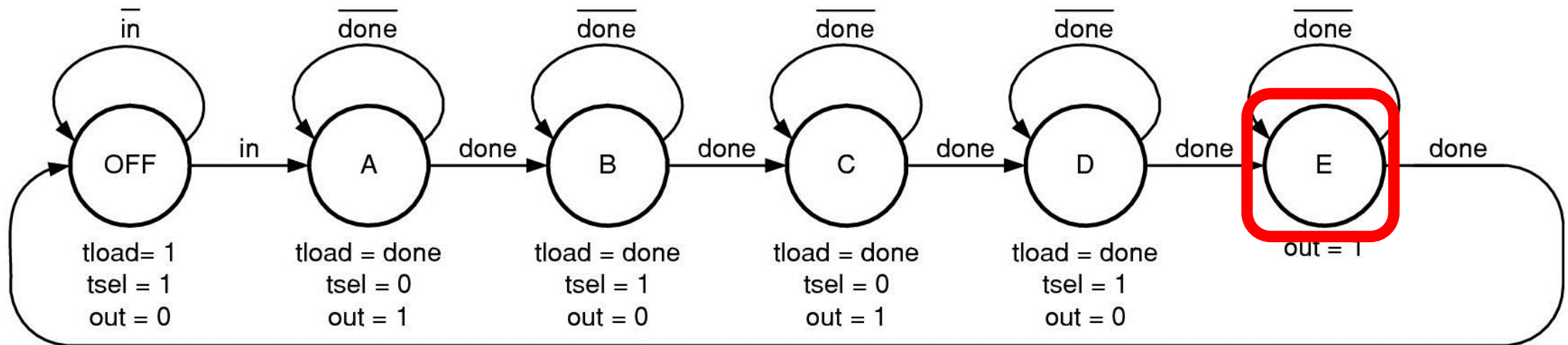
# Example 1: Flashing Light

- First, add a Timer with a Load (Chapter 16) to each of the on-off parts of the flash.



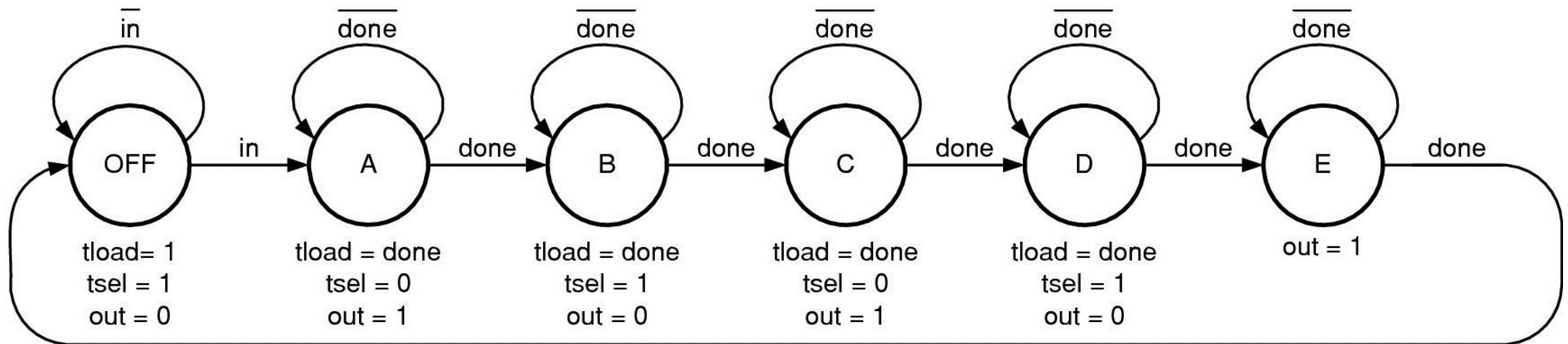
# Example 1: Flashing Light

- tLoad to load the timer
- Tsel to say if it is 6 cycles or 4 Cycles
- Out to say LED on or off.


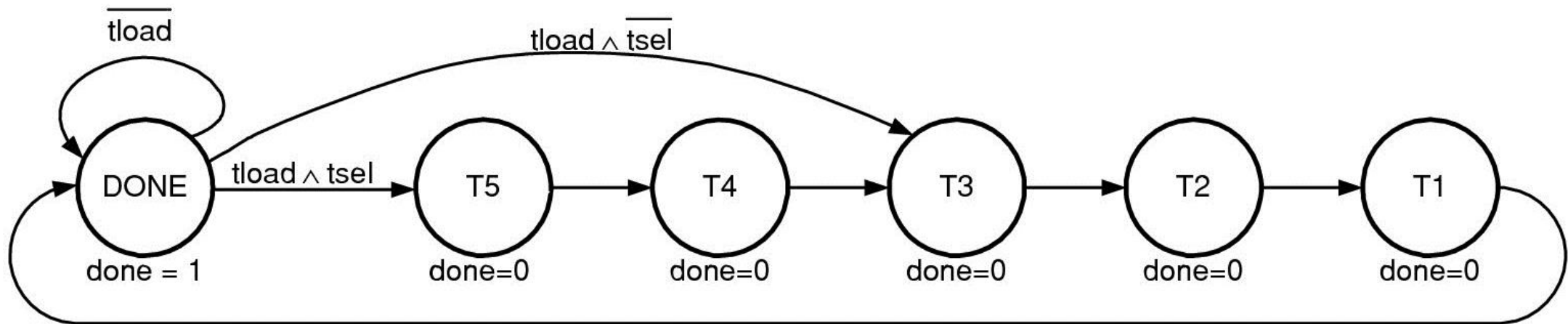
# Example 1: Flashing Light

- Replace the sequence with a timer with a load.




If the Select is high, the LED is on, And count 5,4,3,2,1,0 for 6 hot

If the Select is low, the LED is off, Jump to T3, and the Count is 3,2,1,0 for 4 dark
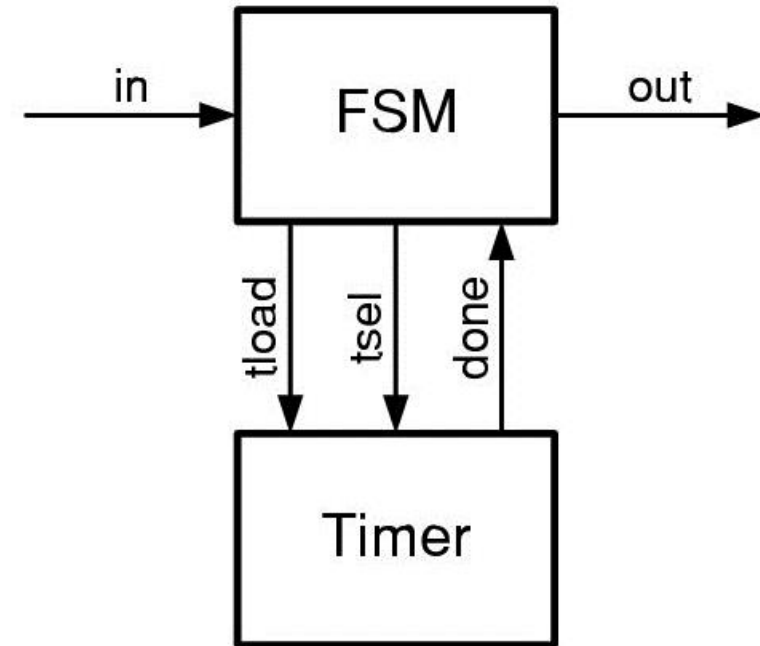
# Example 1: Flashing Light

- The system has two FSM
- The Control FSM says if the light is on or off.
- The Data FSM says how long the light is on or off, with the data being the countdown.





# Example 1: Flashing Light

- Can it be reduced further?

# Example 1: Flashing Light

- Yes.
- A counter can be added.
- The master state machine has three states: off, flash, space
- The Timer state machine will determine the length of the flash or the length of the space.
- The Counter can determine how many times the flash occurs.


# Example 1: Flashing Light

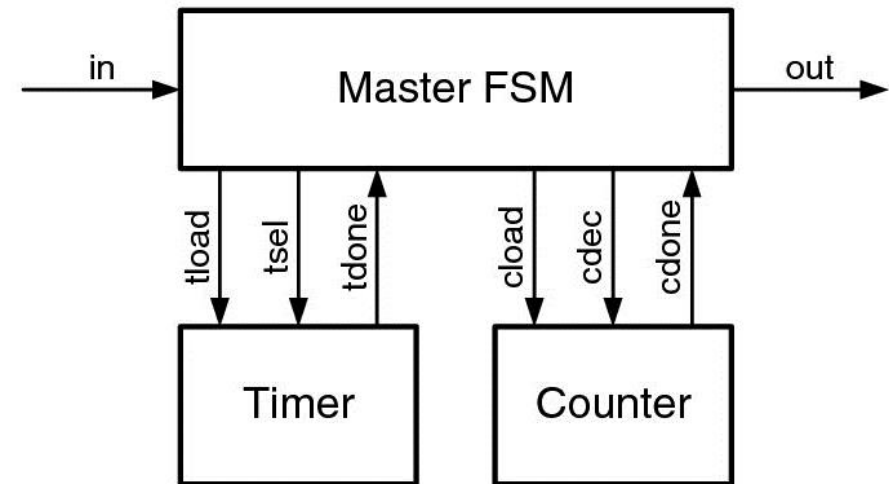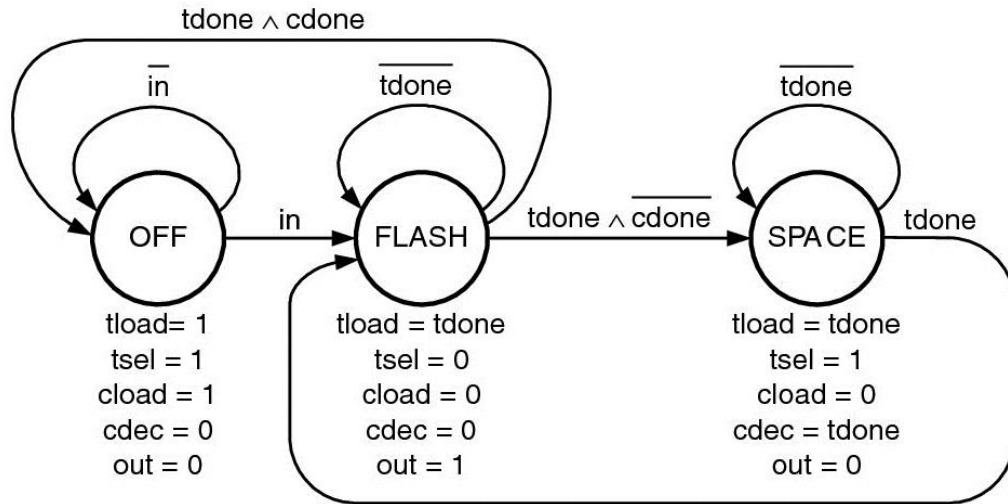

Verilog example available on Blackboard
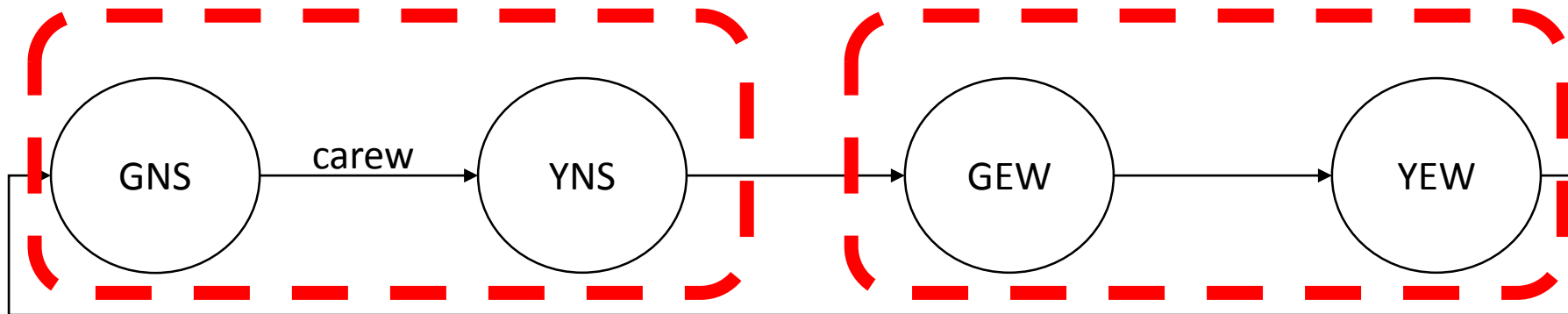
# Back to Traffic Light


- Add a new transition to the Traffic Light problem.
- The original traffic light problem is a single timer instance.
- Could be broken up...well, not really. Too few conditions and states. Maybe 2 states?




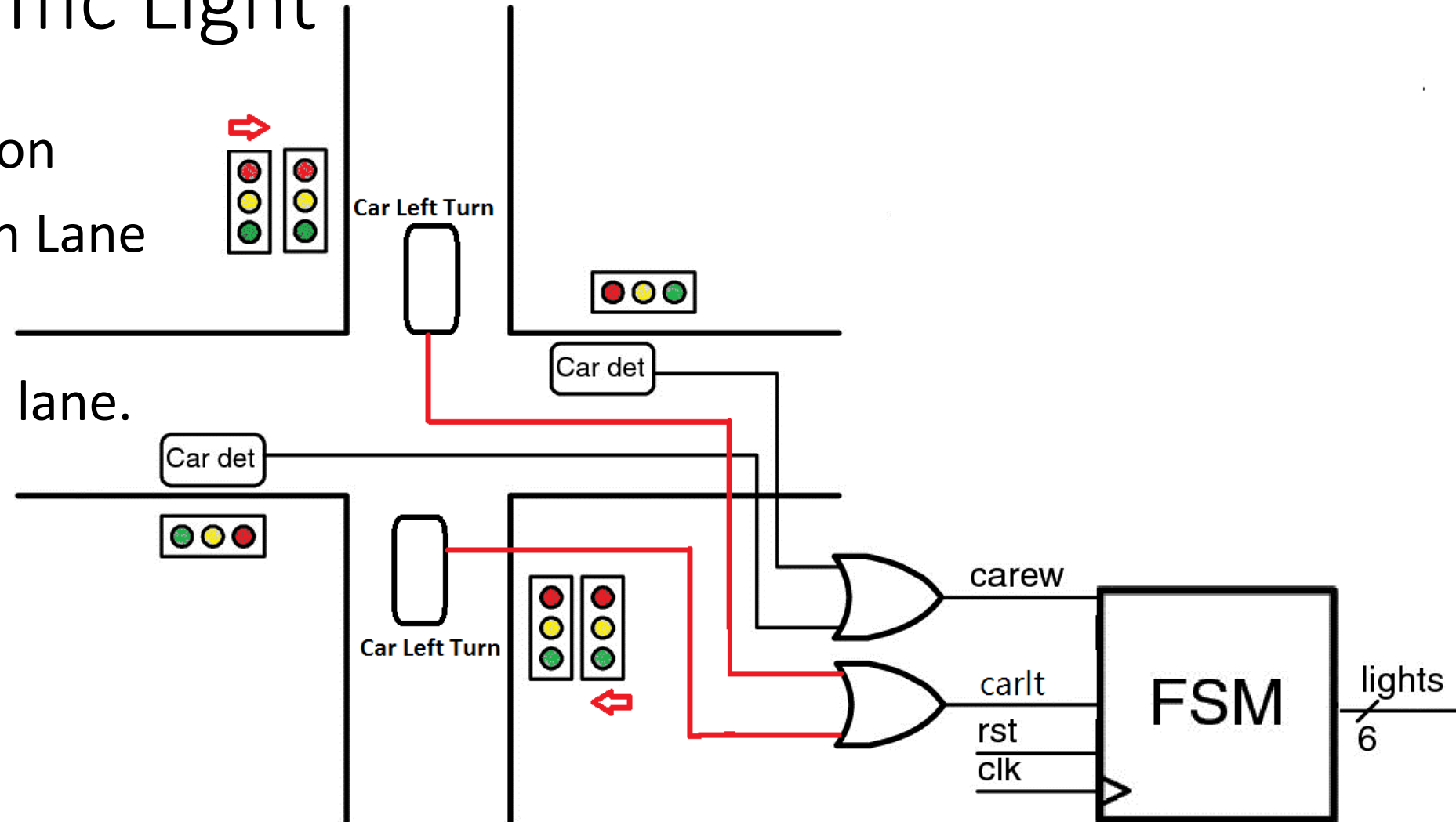
# Back to Traffic Light


- Add a new condition
- Car in the Left Turn Lane
- *carlt*
- in the north-south lane.




# Back to Traffic Light

- Now the problem has:
  - East-West lights
  - North-South Lights
  - Left-Turn Lane Lights
  - A total of 9 lights
- If a car is detected in the left-turn lane is detected
  - Change the north-south light to yellow.
  - Change the north-south light to red.
  - Turn the left turn lane to green.
  - Left Turn has priority.

# Back to Traffic Light

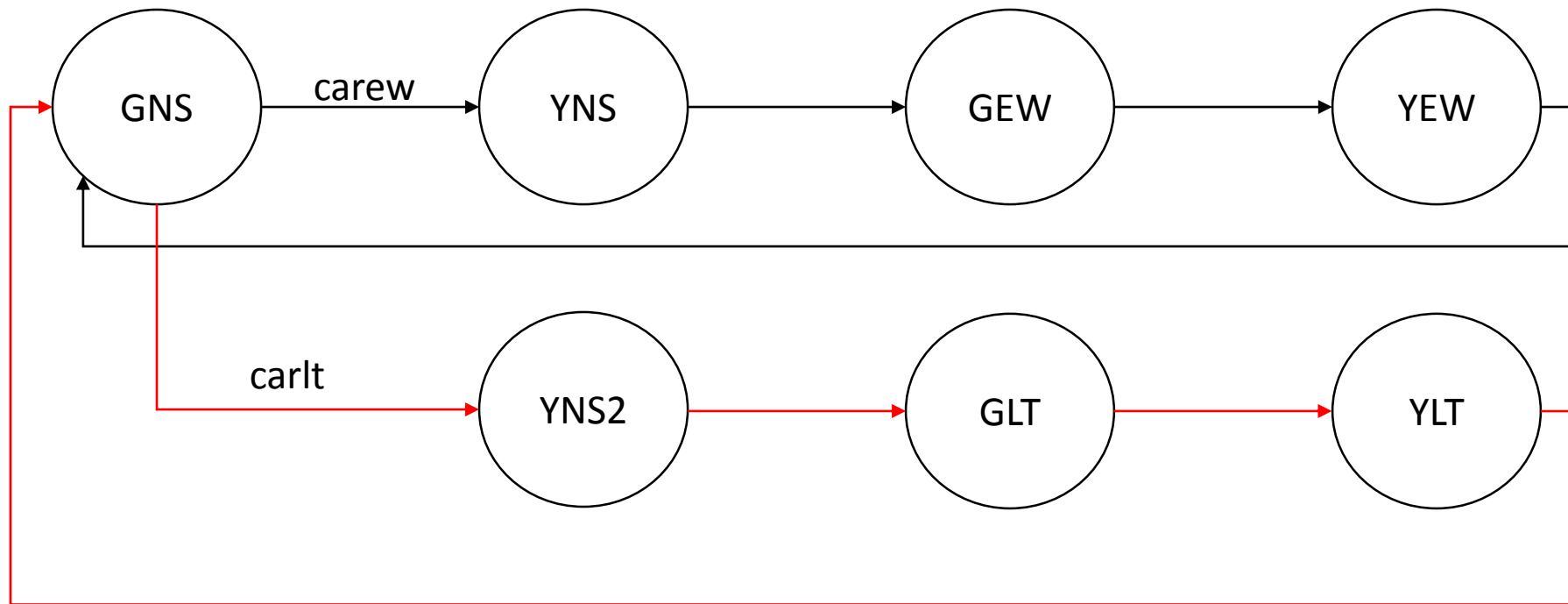

# Back to Traffic Light

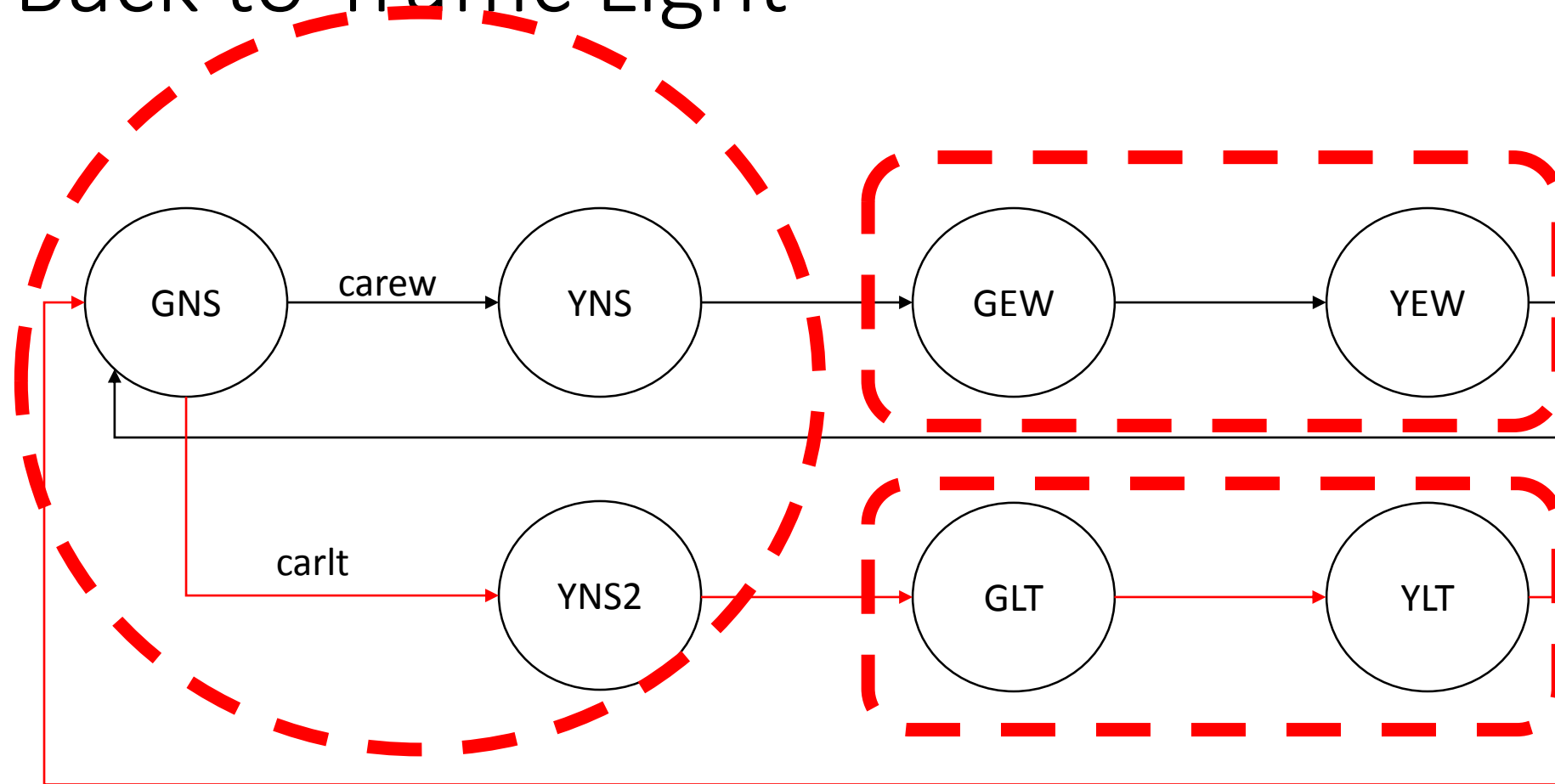

Now, there are three possibilities:


North-South Traffic: NS

East-West Traffic: EW

Left-Turn Traffic: NS

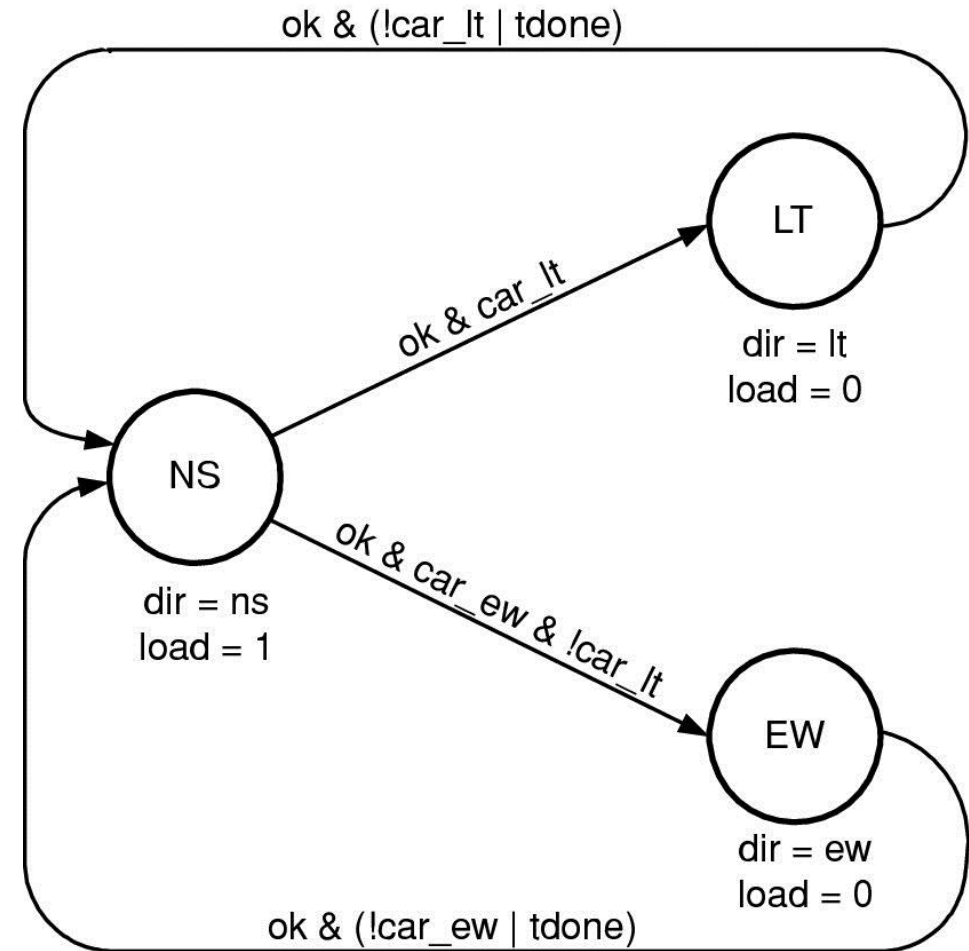
# Back to Traffic Light: Controller FSM

- car\_ew-car detected east-west
- car\_lt-car detected left turn lane
- dir –current direction
- load –load timer command
- ok-a pause, no transition until all is ready
- tdone-timer complete


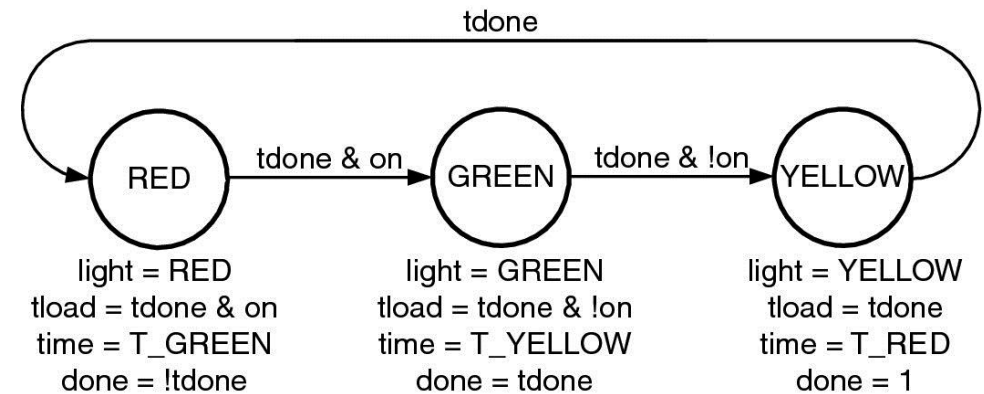
# Back to Traffic Light: Light FSM

- Each timer cycles red, green, yellow
- done=changes on if timer is complete
- light=color
- on-only available if other state is done
- time-next state
- tload-load timer




# Back to Traffic Light: Pieces...


- Components
- Controller FSM
- Light Cycle FSM
- Timer for the Lights
- Timer for the Controller
- Oops...Lights depend on the current state

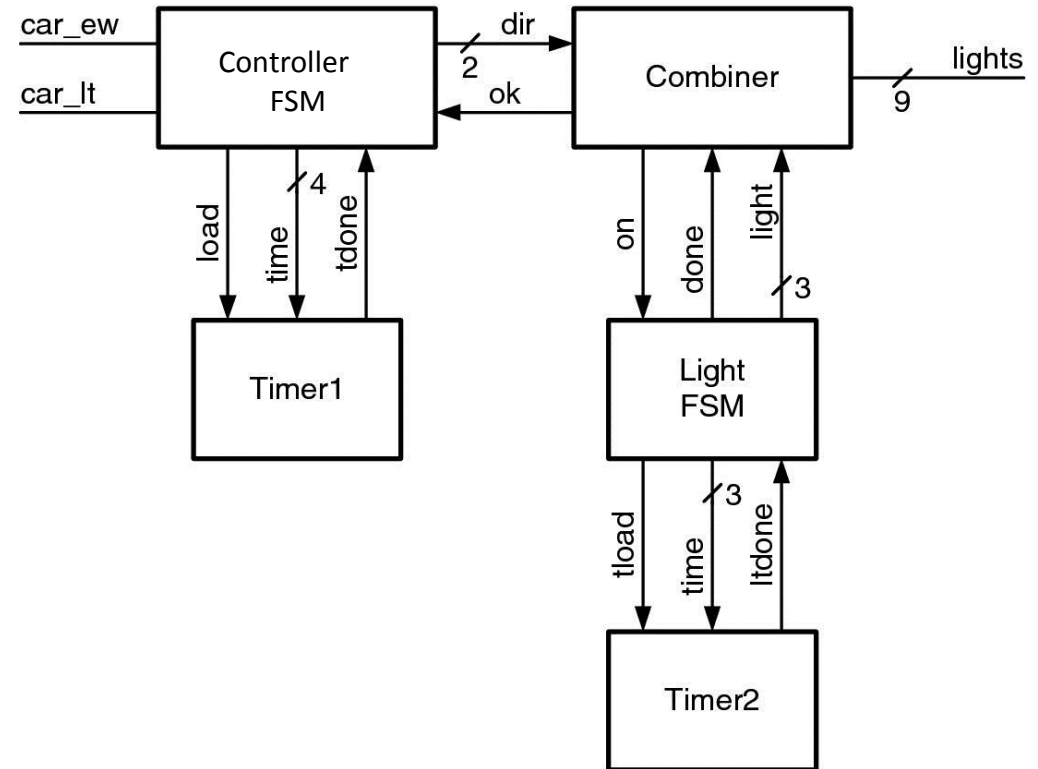
# Back to Traffic Light: Combiner


- The NS to EW to NS is Timer1
- The NS to LT to NS is same Timer1
- The state of the Controller FSM is fed to the Combiner
- Combiner remembers the current direction, from Controller
- Red-Green-Yellow is on Timer2.





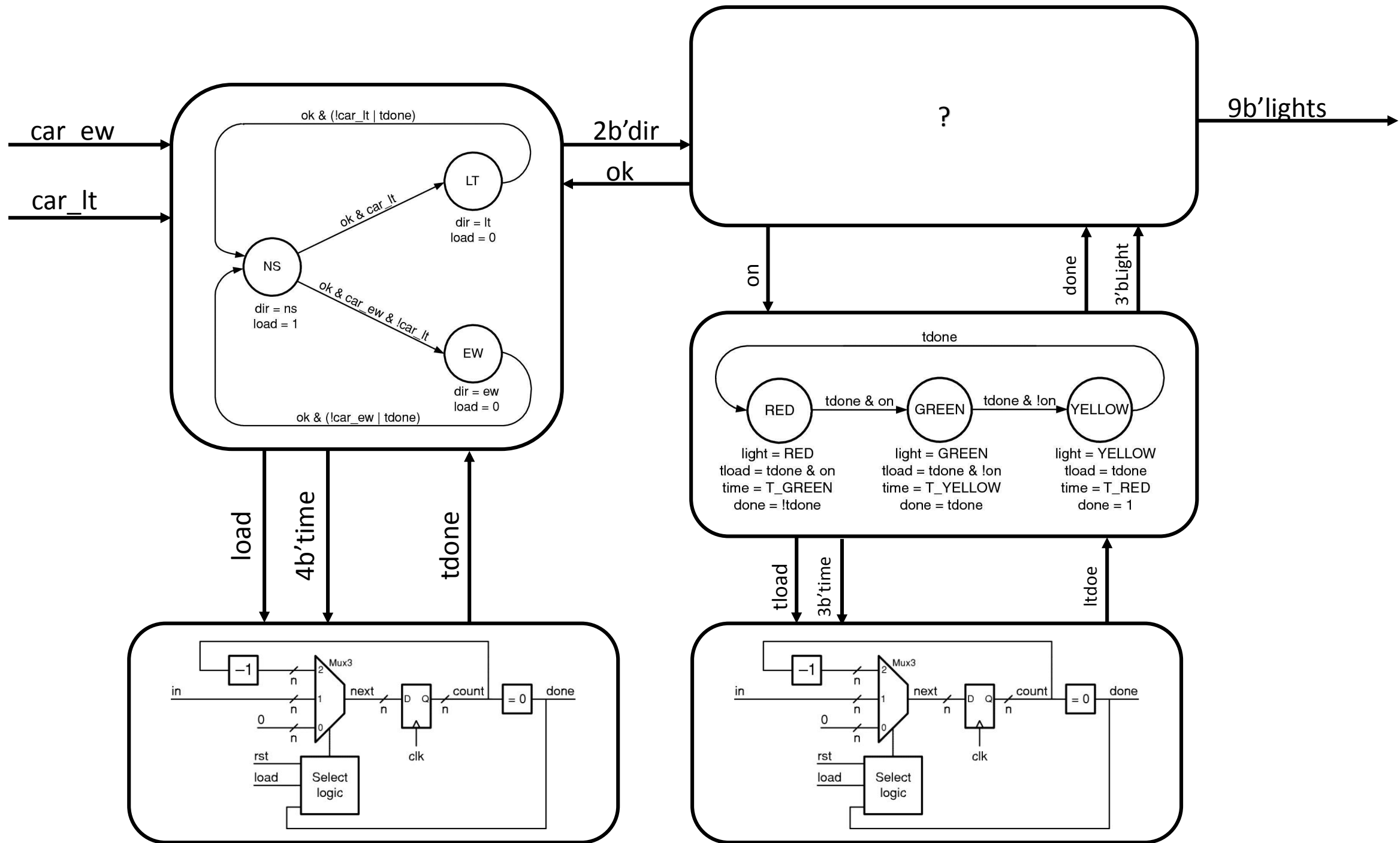

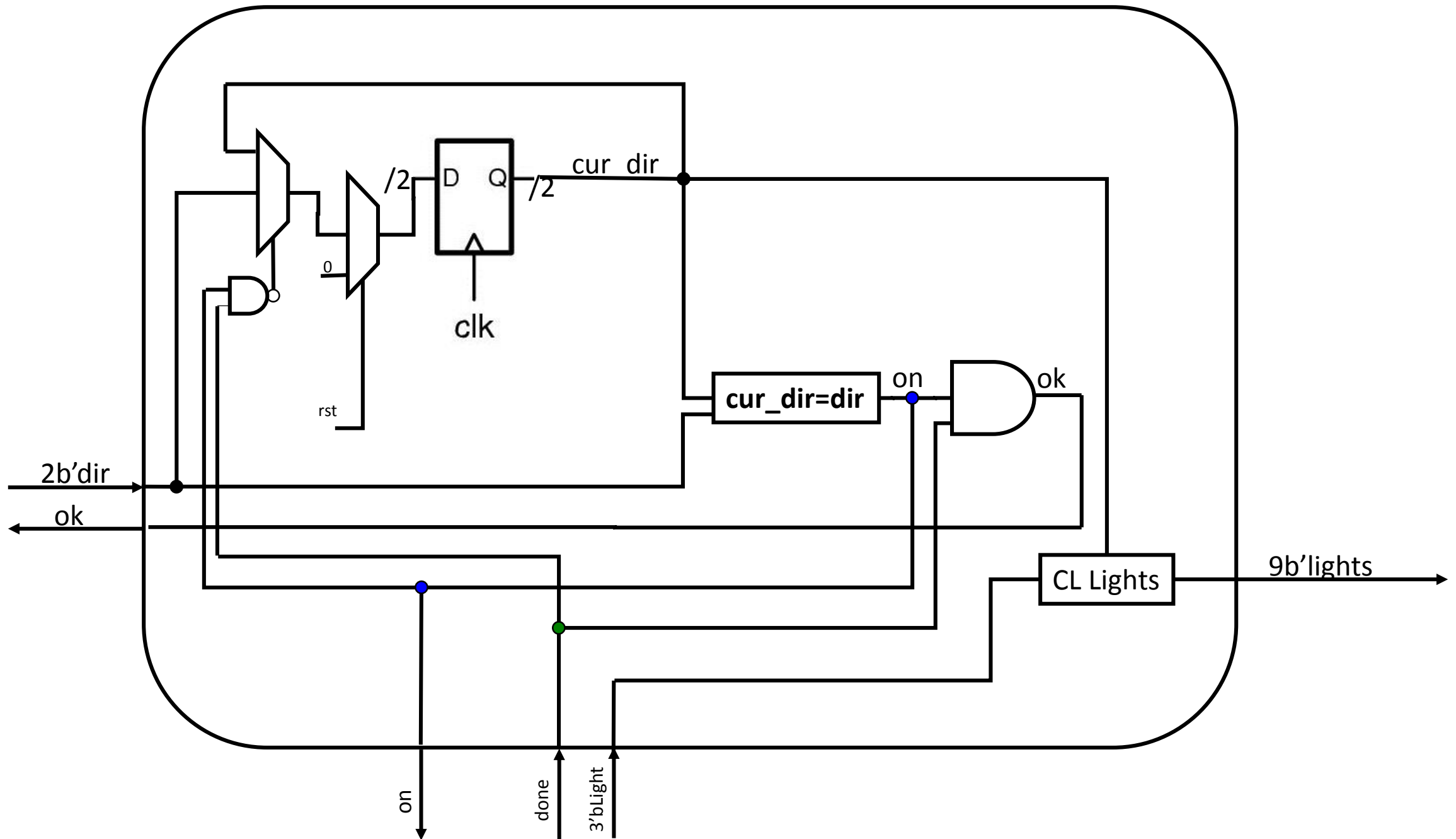

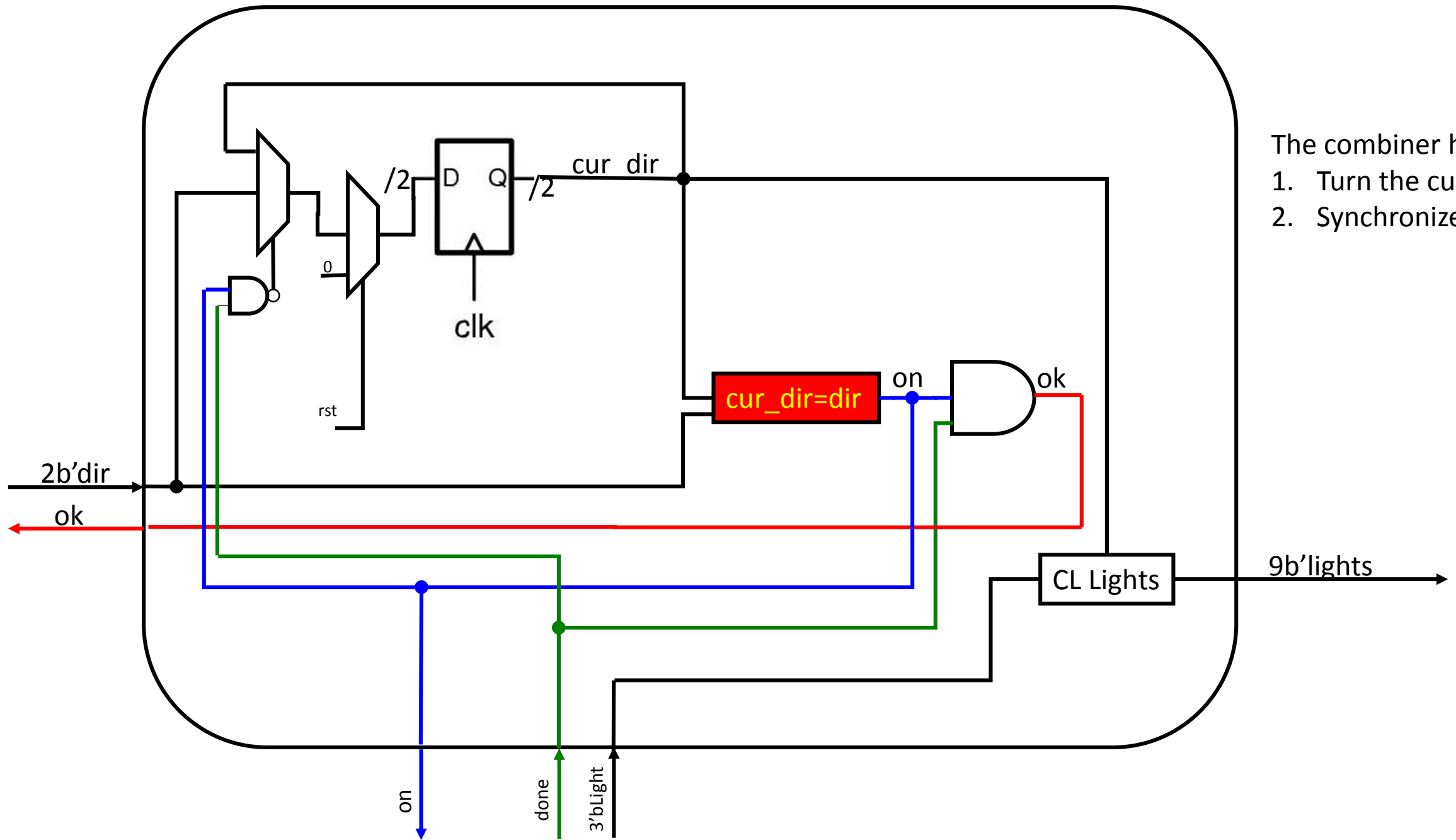

The combiner has two fu

1. Turn the current stat
2. Synchronize the two